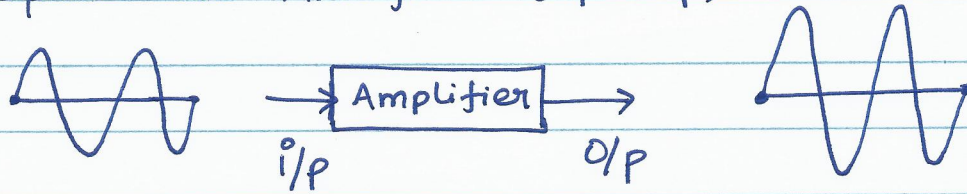



EE 356 - Analog Electronics LAB
LAB 1 - Intro. to Amplifiers.

Savan Suro
①

Operational Amplifiers (Op Amp) \Rightarrow Amplify input Signal



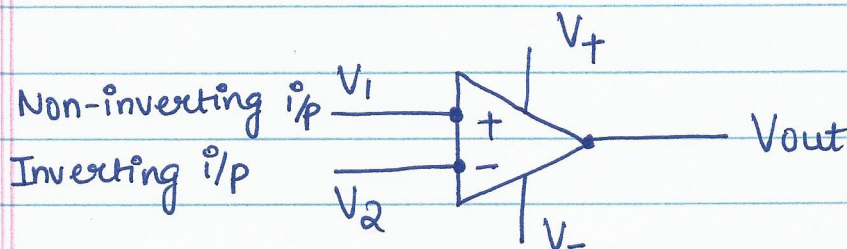In pre digital era, op amps were used to conduct mathematical operations such as addition, subtraction, integration, differentiation, averaging etc.



i/p \Rightarrow input
o/p \Rightarrow output

An op amp is a differential Amplifier. It amplifies the difference between the two signals.

$$\therefore V_{out} = A(V_1 - V_2)$$

$$\Rightarrow A = \frac{V_{out}}{V_1 - V_2}$$

where A is Gain of the amplifier (Op Amp).

when V_2 is grounded, i.e. $V_2 = 0$

then,

$$A = \frac{V_{out}}{V_1}$$

A is called Open loop Gain

with NO FEEDBACK

Similarly, when V_1 is grounded i.e. $V_1 = 0$, then


$$A = \frac{-V_{out}}{V_2}$$

'-ve' sign indicates the inversion of signal.
i.e. 180° phase shift.

* Note that, for a non-inverting amplifier, there is no phase shift. $\Rightarrow 0^\circ$ phase shift

for an inverting amplifier, there is a 180° phase shift \Rightarrow signal looks inverted! (Hence the name)

Non-Inverting Amplifier

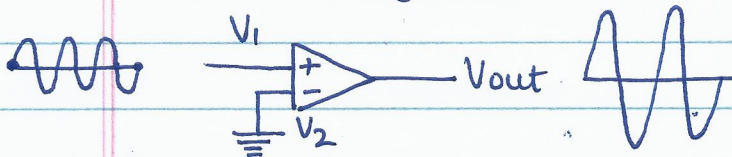


$A = 2$; Amplitude increases by twice

phase diff = 0°

$$V_{out} = A \cdot V_1$$

Inverting Amplifier

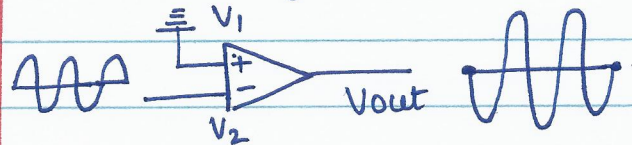

$A = 2$; Amplitude multiplies by two


phase diff = 180°

$$V_{out} = -A \cdot V_2$$

Voltage Transfer

Curve of an Op Amp (Ideal) :-

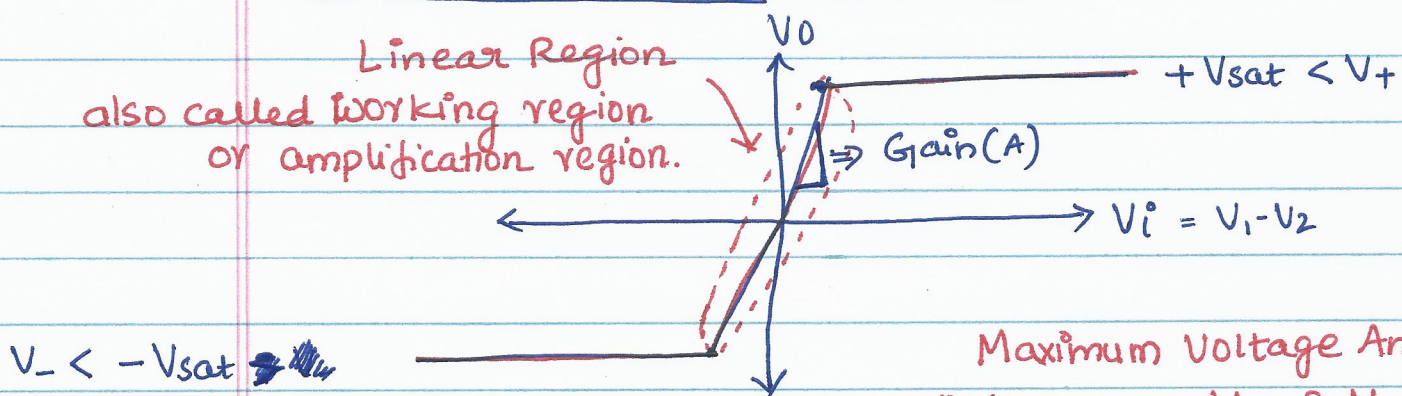Linear Region
also called working region
or amplification region.



Maximum Voltage Amplification
is between V_+ & V_- .

Applications of an Op-Amp :-

- Can be used as
- (1) Active Filter.
 - (2) Oscillators
 - (3) Wave form Converter
 - (4) Analog to Digital Converter (ADC)
 - (5) Digital to Analog Converter (DAC). etc.

IC 741 is ~~very~~ versatile \Rightarrow Many applications.

IDEAL OP-AMP CHARACTERISTICS :-

1. ∞ i/p impedance
2. 0 o/p impedance
3. ∞ open loop gain ($A = \infty$)
4. $V_{out} = 0$ when $V_{in} = 0$

Practically,
(in M- Ω s)
(few Ω s)
($10^4 - 10^6$)
($V_{out} \approx mV$)